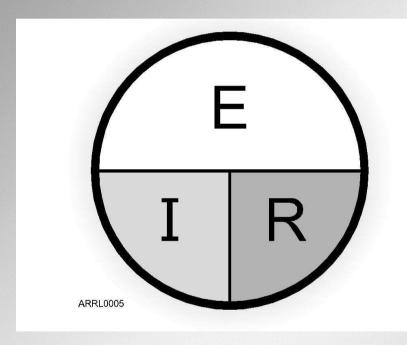
### Technician License Course Chapter 3

Lesson Plan Module 5 –
Ohm's Law, Power, and the Metric
System



#### Ohm's Law



- E represents voltage
  - Units volts (V)
- I represents current
  - Units amperes (A)
- R represents resistance
  - Units ohms  $(\Omega)$

$$R = E / I$$

$$I = E / R$$

$$E = I \times R$$



### Practice Questions



### What formula is used to calculate current in a circuit?

- A. Current (I) equals voltage (E) multiplied by resistance (R)
- B. Current (I) equals voltage (E) divided by resistance (R)
- C. Current (I) equals voltage (E) added to resistance (R)
- D. Current (I) equals voltage (E) minus resistance (R)

  T5D01 HRLM (3-4)



### What formula is used to calculate current in a circuit?

- A. Current (I) equals voltage (E) multiplied by resistance (R)
- B. Current (I) equals voltage (E) divided by resistance (R)
- C. Current (I) equals voltage (E) added to resistance (R)
- D. Current (I) equals voltage (E) minus resistance (R)

  T5D01 HRLM (3-4)



### What formula is used to calculate voltage in a circuit?

- A. Voltage (E) equals current (I) multiplied by resistance (R)
- B. Voltage (E) equals current (I) divided by resistance (R)
- C. Voltage (E) equals current (I) added to resistance (R)
- D. Voltage (E) equals current (I) minus resistance (R)

  T5D02 HRLM (3-4)



### What formula is used to calculate voltage in a circuit?

### A. Voltage (E) equals current (I) multiplied by resistance (R)

- B. Voltage (E) equals current (I) divided by resistance (R)
- C. Voltage (E) equals current (I) added to resistance (R)
- D. Voltage (E) equals current (I) minus resistance (R)

  T5D02 HRLM (3-4)



### What formula is used to calculate resistance in a circuit?

- A. Resistance (R) equals voltage (E) multiplied by current (I)
- B. Resistance (R) equals voltage (E) divided by current (I)
- C. Resistance (R) equals voltage (E) added to current (I)
- D. Resistance (R) equals voltage (E) minus current (I)

  T5D03 HRLM (3-4)



### What formula is used to calculate resistance in a circuit?

- A. Resistance (R) equals voltage (E) multiplied by current (I)
- B. Resistance (R) equals voltage (E) divided by current (I)
- C. Resistance (R) equals voltage (E) added to current (I)
- D. Resistance (R) equals voltage (E) minus current (I)

  T5D03 HRLM (3-4)



# What is the resistance of a circuit in which a current of 3 amperes flows through a resistor connected to 90 volts?

- A. 3 ohms
- B. 30 ohms
- C. 93 ohms
- D. 270 ohms

T5D04 HRLM (3-5)



# What is the resistance of a circuit in which a current of 3 amperes flows through a resistor connected to 90 volts?

- A. 3 ohms
- B. 30 ohms
- C. 93 ohms
- D. 270 ohms

T5D04 HRLM (3-5)



# What is the resistance in a circuit for which the applied voltage is 12 volts and the current flow is 1.5 amperes?

A. 18 ohms

B. 0.125 ohms

C. 8 ohms

D. 13.5 ohms

T5D05 HRLM (3-5)



# What is the resistance in a circuit for which the applied voltage is 12 volts and the current flow is 1.5 amperes?

A. 18 ohms

B. 0.125 ohms

C. 8 ohms

D. 13.5 ohms

T5D05 HRLM (3-5)



## What is the resistance of a circuit that draws 4 amperes from a 12-volt source?

- A. 3 ohms
- B. 16 ohms
- C. 48 ohms
- D. 8 ohms

T5D06 HRLM (3-5)



### What is the resistance of a circuit that draws 4 amperes from a 12-volt source?

#### A. 3 ohms

- B. 16 ohms
- C. 48 ohms
- D. 8 ohms

T5D06 HRLM (3-5)



# What is the current flow in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

- A. 9600 amperes
- B. 200 amperes
- C. 0.667 amperes
- D. 1.5 amperes

T5D07 HRLM (3-5)



# What is the current flow in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

- A. 9600 amperes
- B. 200 amperes
- C. 0.667 amperes
- D. 1.5 amperes

T5D07 HRLM (3-5)



#### What is the current flowing through a 100ohm resistor connected across 200 volts?

- A. 20,000 amperes
- B. 0.5 amperes
- C. 2 amperes
- D. 100 amperes

T5D08 HRLM (3-5)



#### What is the current flowing through a 100ohm resistor connected across 200 volts?

- A. 20,000 amperes
- B. 0.5 amperes
- C. 2 amperes
- D. 100 amperes

T5D08 HRLM (3-5)



#### What is the current flowing through a 24ohm resistor connected across 240 volts?

- A. 24,000 amperes
- B. 0.1 amperes
- C. 10 amperes
- D. 216 amperes

T5D09 HRLM (3-5)



#### What is the current flowing through a 24ohm resistor connected across 240 volts?

- A. 24,000 amperes
- B. 0.1 amperes
- C. 10 amperes
- D. 216 amperes

T5D09 HRLM (3-5)



## What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

A. 1 volt

**B.** 0.25 volts

C. 2.5 volts

D. 1.5 volts

T5D10 HRLM (3-5)



## What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

#### A. 1 volt

**B.** 0.25 volts

C. 2.5 volts

D. 1.5 volts

T5D10 HRLM (3-5)



## What is the voltage across a 10-ohm resistor if a current of 1 ampere flows through it?

A. 1 volt

B. 10 volts

C. 11 volts

D. 9 volts

T5D11 HRLM (3-5)



## What is the voltage across a 10-ohm resistor if a current of 1 ampere flows through it?

A. 1 volt

B. 10 volts

C. 11 volts

D. 9 volts

T5D11 HRLM (3-5)



## What is the voltage across a 10-ohm resistor if a current of 2 amperes flows through it?

A. 8 volts

B. 0.2 volts

C. 12 volts

D. 20 volts

T5D12 HRLM (3-5)



### What is the voltage across a 10-ohm resistor if a current of 2 amperes flows through it?

A. 8 volts

B. 0.2 volts

C. 12 volts

D. 20 volts

T5D12 HRLM (3-5)



# Power - Electrons Doing Work and Expending Energy

- Any time energy is expended, power is consumed.
- Electrons moving through resistance expend electrical energy and consume power.
- Power is the rate at which energy is consumed.
- Power is measured in units of watts (W).


### Power Equation

Power is calculated as the product of voltage and current

$$P = E \times I$$

$$E = P/I$$

$$I = P / E$$

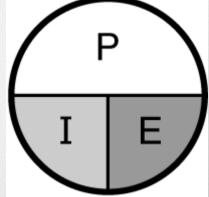

• Like Ohm's Law, if you know two of the values, you can calculate the third.



### Practice Questions



## Electrical power is measured in which of the following units?

- A. Volts
- B. Watts
- C. Ohms
- D. Amperes

T5A02 HRLM (3-5)



## Electrical power is measured in which of the following units?

- A. Volts
- **B.** Watts
- C. Ohms
- D. Amperes

T5A02 HRLM (3-5)



## Which term describes the rate at which electrical energy is used?

- A. Resistance
- B. Current
- C. Power
- D. Voltage

T5A10 HRLM (3-5)



## Which term describes the rate at which electrical energy is used?

- A. Resistance
- B. Current
- C. Power
- D. Voltage

T5A10 HRLM (3-5)



## What is the formula used to calculate electrical power in a DC circuit?

- A. Power (P) equals voltage (E) multiplied by current (I)
- B. Power (P) equals voltage (E) divided by current (I)
- C. Power (P) equals voltage (E) minus current (I)
- D. Power (P) equals voltage (E) plus current (I)

T5C08 HRLM (3-5)



## What is the formula used to calculate electrical power in a DC circuit?

- A. Power (P) equals voltage (E) multiplied by current (I)
- B. Power (P) equals voltage (E) divided by current (I)
- C. Power (P) equals voltage (E) minus current (I)
- D. Power (P) equals voltage (E) plus current (I)

T5C08 HRLM (3-5)



# How much power is being used in a circuit when the applied voltage is 13.8 volts DC and the current is 10 amperes?

A. 138 watts

B. 0.7 watts

C. 23.8 watts

D. 3.8 watts

T5C09 HRLM (3-5)



# How much power is being used in a circuit when the applied voltage is 13.8 volts DC and the current is 10 amperes?

#### **A. 138 watts**

B. 0.7 watts

C. 23.8 watts

D. 3.8 watts

T5C09 HRLM (3-5)



# How much power is being used in a circuit when the applied voltage is 12 volts DC and the current is 2.5 amperes?

A. 4.8 watts

B. 30 watts

C. 14.5 watts

D. 0.208 watts

T5C10 HRLM (3-5)



# How much power is being used in a circuit when the applied voltage is 12 volts DC and the current is 2.5 amperes?

A. 4.8 watts

B. 30 watts

C. 14.5 watts

D. 0.208 watts

T5C10 HRLM (3-5)



## How many amperes are flowing in a circuit when the applied voltage is 12 volts DC and the load is 120 watts?

- A. 0.1 amperes
- B. 10 amperes
- C. 12 amperes
- D. 132 amperes

T5C11 HRLM (3-5)



## How many amperes are flowing in a circuit when the applied voltage is 12 volts DC and the load is 120 watts?

- A. 0.1 amperes
- B. 10 amperes
- C. 12 amperes
- D. 132 amperes

T5C11 HRLM (3-5)



#### Metric Prefixes

Table 2-1 International System of Units (SI)—Metric Units			
Prefix	Symbol	Multiplication Factor	
Tera	Т	$10^{12} = 1,000,000,000,000$	
Giga	G	$10^9 = 1,000,000,000$	
Mega	М	$10^6 = 1,000,000$	
Kilo	k	$10^3 = 1000$	
Hecto	h	$10^2 = 100$	
Deca	da	$10^1 = 10$	
Deci	d	$10^{-1} = 0.1$	
Centi	С	$10^{-2} = 0.01$	
Milli	m	$10^{-3} = 0.001$	
Micro	μ	$10^{-6} = 0.000001$	
Nano	n	$10^{-9} = 0.000000001$	
Pico	р	$10^{-12} = 0.000000000001$	



### **Electrical Units**

Electrical Units and Their Namesakes			
Unit	Measures	Named for	
Ampere	Current	Andree Marie Ampere (1775 – 1836)	
Coulomb	Charge	Charles Augustin Coulomb (1736 - 1806)	
Farad	Capacitance	Michael Faraday (1791 - 1867)	
Henry	Inductance	Joseph Henry (1797 - 1878)	
Hertz	Frequency	Heinrich Hertz (1857 – 1894)	
Ohm	Resistance	George Simon Ohm (1787 - 1854)	
Watt	Power	James Watt (1736 - 1819)	
Volt	Voltage	Alessandro Giuseppe Antonio Anastasio Volta (1745 – 1827)	



#### How many milliamperes is 1.5 amperes?

- A. 15 milliamperes
- B. 150 milliamperes
- C. 1,500 milliamperes
- D. 15,000 milliamperes

T5B01 HRLM (2-2)



#### How many milliamperes is 1.5 amperes?

- A. 15 milliamperes
- B. 150 milliamperes
- C. 1,500 milliamperes
- D. 15,000 milliamperes

T5B01 HRLM (2-2)



### What is another way to specify a radio signal frequency of 1,500,000 hertz?

A. 1500 kHz

B. 1500 MHz

C. 15 GHz

D. 150 kHz

T5B02 HRLM (2-2)



### What is another way to specify a radio signal frequency of 1,500,000 hertz?

A. 1500 kHz

B. 1500 MHz

C. 15 GHz

D. 150 kHz

T5B02 HRLM (2-2)



#### How many volts are equal to one kilovolt?

- A. One one-thousandth of a volt
- B. One hundred volts
- C. One thousand volts
- D. One million volts

T5B03 HRLM (2-2)



#### How many volts are equal to one kilovolt?

- A. One one-thousandth of a volt
- B. One hundred volts
- C. One thousand volts
- D. One million volts

T5B03 HRLM (2-2)



#### How many volts are equal to one microvolt?

- A. One one-millionth of a volt
- B. One million volts
- C. One thousand kilovolts
- D. One one-thousandth of a volt

T5B04 HRLM (2-2)



#### How many volts are equal to one microvolt?

- A. One one-millionth of a volt
- B. One million volts
- C. One thousand kilovolts
- D. One one-thousandth of a volt

T5B04 HRLM (2-2)



### Which of the following is equivalent to 500 milliwatts?

A. 0.02 watts

B. 0.5 watts

C. 5 watts

D. 50 watts

T5B05 HRLM (2-2)



### Which of the following is equivalent to 500 milliwatts?

A. 0.02 watts

B. 0.5 watts

C. 5 watts

D. 50 watts

T5B05 HRLM (2-2)



# If an ammeter calibrated in amperes is used to measure a 3000-milliampere current, what reading would it show?

- A. 0.003 amperes
- B. 0.3 amperes
- C. 3 amperes
- D. 3,000,000 amperes

T5B06 HRLM (2-2)



# If an ammeter calibrated in amperes is used to measure a 3000-milliampere current, what reading would it show?

- A. 0.003 amperes
- B. 0.3 amperes
- C. 3 amperes
- D. 3,000,000 amperes

T5B06 HRLM (2-2)



## If a frequency readout calibrated in megahertz shows a reading of 3.525 MHz, what would it show if it were calibrated in kilohertz?

A. 0.003525 kHz

B. 35.25 kHz

C. 3525 kHz

D. 3,525,000 kHz

T5B07 HRLM (2-2)



## If a frequency readout calibrated in megahertz shows a reading of 3.525 MHz, what would it show if it were calibrated in kilohertz?

A. 0.003525 kHz

B. 35.25 kHz

C. 3525 kHz

D. 3,525,000 kHz

T5B07 HRLM (2-2)



## How many microfarads are 1,000,000 picofarads?

- A. 0.001 microfarads
- B. 1 microfarad
- C. 1000 microfarads
- D. 1,000,000,000 microfarads

T5B08 HRLM (2-2)



## How many microfarads are 1,000,000 picofarads?

- A. 0.001 microfarads
- B. 1 microfarad
- C. 1000 microfarads
- D. 1,000,000,000 microfarads

T5B08 HRLM (2-2)



### Which of the following frequencies is equal to 28,400 kHz?

A. 28.400 MHz

B. 2.800 MHz

C. 284.00 MHz

D. 28.400 kHz

T5B12 HRLM (2-2)



### Which of the following frequencies is equal to 28,400 kHz?

A. 28,400 MHz

B. 2.800 MHz

C. 284.00 MHz

D. 28.400 kHz

T5B12 HRLM (2-2)



### If a frequency readout shows a reading of 2425 MHz, what frequency is that in GHz?

A. 0.002425 GHz

B. 24.25 GHz

C. 2.425 GHz

D. 2425 GHz

T5B13 HRLM (2-2)



### If a frequency readout shows a reading of 2425 MHz, what frequency is that in GHz?

A. 0.002425 GHz

B. 24.25 GHz

C. 2.425 GHz

D. 2425 GHz

T5B13 HRLM (2-2)

